

Logic

EE599-001 & EE699-010, Spring 2026

Hank Dietz

<http://aggregate.org/hankd/>

Quantum is Programmed at the (Qu)Bit/Gate Level

- Gate-level optimization is critical
 - Very few qubits
 - Very limited gate sequence depth
 - Additional constraints on gates
- Quantum gates
 - Different; optimization is harder
 - Some quantum gates don't have conventional analogs (e.g., $\sqrt{\text{NOT}}$); we'll start with the ones that do


Digital Logic & Optimization

- Conventional gates
 - Basic gate types, fanout
 - Logic optimization
- Adiabatic/Reversible logic
 - Gate types and mechanisms
 - No fanout; ancilla
 - Logic optimization
- A little Verilog project...

Conventional Gates: NOT

- NOT (A) , !A, ~A


A		Q
0		1
1		0

 

Conventional Gates: AND

- **AND (A, B), A&B, A*B, AB**


A	B		Q
0	0		0
0	1		0
1	0		0
1	1		1

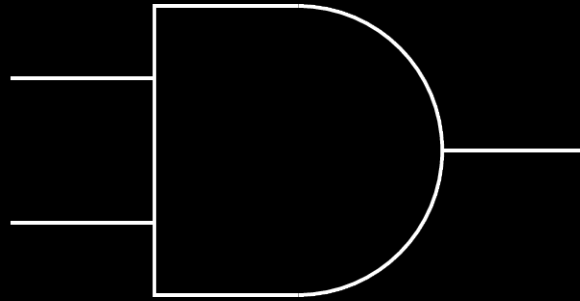

Conventional Gates: OR

- $\text{OR}(A, B)$, $A \mid B$, $A+B$

A	B		Q
0	0		0
0	1		1
1	0		1
1	1		1

 

Logic Optimization

- Sum of Products form
 - OR over ANDs, with NOTs
 - Rule-based simplifier here:
<https://www.boolean-algebra.com/>
- Karnaugh maps
- Quine-McClusky:
<https://www.mathematik.uni-marburg.de/~thormae/lectures/ti1/code/qmc/>
- Espresso (in Python EDA):
<https://pyeda.readthedocs.io/en/latest/211m.html>
- Don't actually optimize for 2-input gates...

We'll Be Using Verilog...

- IEEE 1364-2005
- My slides about Verilog

<https://aggregate.org/CPE380/slidesS26verilog.pdf>

- Various Verilog materials online, e.g.:

<http://www.asic-world.com/verilog/>

- Icarus Verilog

https://en.wikipedia.org/wiki/Icarus_Verilog

- My CGI interface to Icarus Verilog

<https://aggregate.org/cgi-bin/iver.cgi>

We'll Be Using Verilog...

- IEEE 1364-2005
- **Verilog HDL** by Samir Palnitkar,
ISBN-978-0132599702
- Various Verilog materials online, e.g.:
<http://www.asic-world.com/verilog/>
- Icarus Verilog
https://en.wikipedia.org/wiki/Icarus_Verilog
- My CGI interface to Icarus Verilog
<https://aggregate.org/cgi-bin/iver.cgi>

We'll Be Using Verilog...

- We will use Verilog to implement a gate-level circuit design & test it
- Test will be exhaustive, using an oracle
- Let's run through what that looks like with a simple example from CPE380:
a **ripple carry adder**
- First fixed size, then parametric...

A 1-Bit Half Adder (HA)

```
// Half Adder
module ha(sum, cout, a, b);
output sum, cout;
input a, b;
assign sum = a ^ b;      // sum
assign cout = a & b;     // cout
endmodule
```

A 1-Bit Half Adder (HA)

```
// Half Adder
module ha(sum, cout, a, b);
output sum, cout;
input a, b;
xor(sum, a, b);           // sum
and(cout, a, b);          // cout
endmodule
```

A 1-Bit Full Adder (FA)

```
// Full Adder
module fa(sum, cout, a, b, cin);
output sum, cout;
input a, b, cin;
wire aorb, gen, prop;
xor(sum, a, b, cin);      // sum
and(gen, a, b);           // generate
or(aorb, a, b);           // propagate
and(prop, aorb, cin);
or(cout, gen, prop);      // cout
endmodule
```

A 1-Bit Full Adder (FA)

```
`define CSWAP(C,A,B) {A,B}=(C?{B,A}:{A,B})

// Full Adder
module cswapfa(sum, cout, ain, bin, cin);
input ain, bin, cin;
output reg sum, cout; // total 5 registers
reg a, b, g;
always @ (*) begin
    sum = 0; cout = cin; a = ain; b = bin; g = 1;
    `CSWAP(a, sum, g);
    `CSWAP(b, sum, g);
    `CSWAP(cout, sum, g);
    `CSWAP(sum, cout, g);
    `CSWAP(b, cout, g);
end
endmodule
```

A 1-Bit Full Adder (FA)

```
`define CSWAP(C,A,B) {A,B}=(C?{B,A}:{A,B})

// CSWAP Full Adder
module cswapfa(sum, cout, a, b, cin);
input ain, bin, cin;
output reg sum, cout; // total 3 writable registers
reg g;
always @ (*) begin
    sum = 0; cout = cin; g = 1;
    `CSWAP(a, sum, g);
    `CSWAP(b, sum, g);
    `CSWAP(cout, sum, g);
    `CSWAP(sum, cout, g);
    `CSWAP(b, cout, g);
end
endmodule
```

An 8-Bit Ripple Carry Adder

```
// Ripple carry addition, 8-bit
module add8(sum, cout, a, b, cin);
output [7:0] sum;
output cout;
input [7:0] a, b;
input cin;
wire [6:0] lcout;
fa fa0(sum[0], lcout[0], a[0], b[0], cin),
   fa1(sum[1], lcout[1], a[1], b[1], lcout[0]),
   fa2(sum[2], lcout[2], a[2], b[2], lcout[1]),
   fa3(sum[3], lcout[3], a[3], b[3], lcout[2]),
   fa4(sum[4], lcout[4], a[4], b[4], lcout[3]),
   fa5(sum[5], lcout[5], a[5], b[5], lcout[4]),
   fa6(sum[6], lcout[6], a[6], b[6], lcout[5]),
   fa7(sum[7], cout, a[7], b[7], lcout[6]);
endmodule
```


Let's Test It: testbench

```
module testbench;
reg [7:0] a, b, refsum; wire [7:0] sum;
reg cin, refcout; wire cout; integer tested=0, wrong=0;

add8 uut(sum, cout, a, b, cin);          // unit under test

initial begin a=0; repeat (256) begin b=0;
  repeat (256) begin cin=0; repeat (2) #1 begin
    {refcout, refsum} = a + b + cin;  // oracle
    tested=tested+1;
    if ((refcout != cout) || (refsum != sum)) begin
$display("Wrong: %d+%d+%d is {%d,%d}, but got {%d,%d}",
  a, b, cin, refcout, refsum, cout, sum);
    wrong=wrong+1;
  end cin=1; end b = b + 1; end a = a + 1; end
$display("%d cases tested, %d wrong", tested, wrong);
end endmodule
```

Let's Really Test It...

- Can run it here:
<http://aggregate.org/EE380/alurripple8.html>
- Notice that this is an **exhaustive test**
 - All 131,072 cases are tried ($2^8 \times 2^8 \times 2$)
 - Exhaustive testing quickly becomes less feasible as number of input bits grows

A Parametric Ripple Adder

```
// Ripple carry addition, BITS-bit
module add(sum, cout, a, b, cin);
parameter BITS=8;
output [BITS-1:0] sum;
output cout;
input [BITS-1:0] a, b;
input cin;
wire [BITS:0] c; // temporary (local) wires

genvar i;
generate for (i=0; i<BITS; i=i+1) begin:fas
    // full adders named fas[i].myfa
    fa myfa(sum[i], c[i+1], a[i], b[i], c[i]);
end endgenerate

assign c[0] = cin; // first carry in
assign cout = c[BITS]; // last carry out
endmodule
```

Let's Test That One Too...

- Can run it here:
<http://aggregate.org/EE380/alurippleBITS.html>
- Notice that the entire Verilog program is **just one line longer** than the 8-bit-only version
- This version essentially **generates the exact same gates**; there's no hardware cost to being parametric

All 16 Functions of 2 Inputs


- Enumerating values in order of {B,A}:

0000	0	1000	$\neg(A \vee B)$
0001	$A \wedge B$	1001	$\neg(A \wedge B)$, $A \neq B$
0010	$A \wedge \neg B$	1010	$\neg B$
0011	A	1011	$A \vee \neg B$, $A \geq B$
0100	$B \wedge \neg A$	1100	$\neg A$
0101	B	1101	$B \vee \neg A$, $B \geq A$
0110	$A \vee B$, $A \neq B$	1110	$\neg(A \wedge B)$
0111	$A \vee B$	1111	1

Conventional Gates: XOR

- XOR (A, B), $A \oplus B$, $A \neq B$, $A+B$, odd parity



A	B		Q
0	0		0
0	1		1
1	0		1
1	1		0

 

Conventional Gates: NAND

- **NAND (A , B) is NOT (AND (A , B))**

A	B		Q
0	0		1
0	1		1
1	0		1
1	1		0

 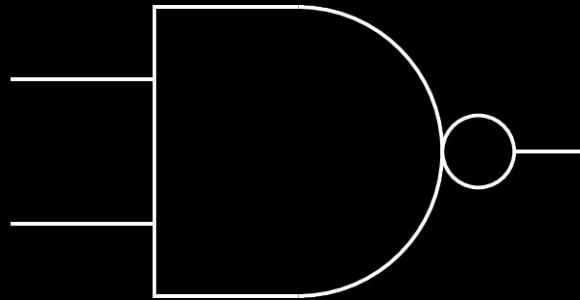


- Note TTL Totem Pole output





Conventional Gates: NOR

- $\text{NOR}(A, B)$ is $\text{NOT}(\text{OR}(A, B))$


A	B		Q
0	0		1
0	1		0
1	0		0
1	1		0

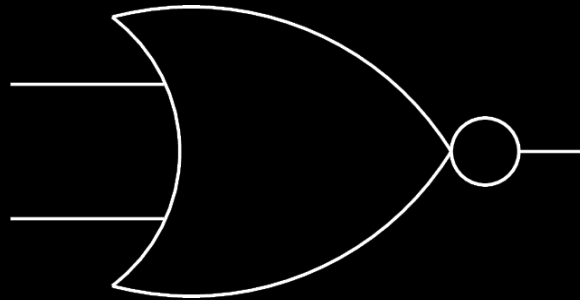

Constructing XOR

    

BDD Analysis/Optimization

 


- **BDD** (Binary Decision Diagram) is commonly used for proofs and logic optimization
- **Biddy** is a library for BDD optimization
<https://aggregate.org/cgi-bin/biddy.cgi>

BDD Gate is **ITE** (If-Then-Else)

- $\text{ITE}(S, B, A)$ is $\text{MUX}(S, A, B), (S ? B : A)$

S	A	B		Q
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		0
1	1	1		1

 

Conventional Gates: ITE

- **ITE (S, B, A)** is a universal gate:

NOT (A) **(A?0:1)**


AND (A, B) **(A?B:0)**

OR (A, B) **(A?1:B)**

XOR (A, B) **(A? (B?0:1) :B)**

- Also used as BDD (Binary Decision Diagram)

BitC Language & Compiler

 


- **BitC** is a C dialect created for **KY Architecture Nanocontrollers: KITE (KY If-Then-Else)**

<https://aggregate.org/KYARCH/>

- **bitcc** is the BitC compiler generating ITEs

<https://aggregate.org/cgi-bin/bitcc.cgi>

A BitC Example

 

- `int:4 a; int:2 b, c; a=b*c;`
- `[r0]=0, [r1]=1, [r5:r2]=a, [r7:r6]=b, [r9:r8]=b`

<https://aggregate.org/cgi-bin/bitcc.cgi>

ITEs in Verilog

- Verilog has the `? :` operator
 - We want to *sequence* gates, so we'll use `regs` and assignments in an `always`
 - Make a `SITE` macro: Store ITE
- Our example multiplies 3-bit numbers
 - `int:3 a,b,c; a=b*c;`
<https://aggregate.org/cgi-bin/bitcc.cgi>
 - Here's the Verilog code:
<https://aggregate.org/QC/sitemul.html>

Adiabatic Logic

- Thermodynamically reversible gates
 - Fredkin & Toffoli, 1978: used caps+inductors
 - Hall 1992 & Merkle 1992: 1st reversible comb.
 - Younis & Knight, 1993: 1st reversible FSM
 - Group at MIT, 1995-1999: Pendulum, etc.
 - More in Flordia, Notre Dame, UK, etc.;
- Spring 2019 CPE480 AXA:
<https://aggregate.org/EE480/axa.html>
- Gates can operate forward or reverse...
can even build instruction set to do that

Reversible Instructions

- Have inverses...
 - XOR (but NOT AND, OR!)
 - Rotates (but NOT Shifts!)
 - Add, Subtract
 - Exchange (but NOT Store or Load!)
 - Jumps that note where they came from (land)
- $A \oplus B$ is reversible, but $A \oplus A$ is NOT
- Using only such ops, code can execute forward or backward

Energy Recovery

- Power supply is phased (i.e., a clock)
 - Fanout == 1
 - Send energy forward, then recover it:
think sending +1, then recovering -1
 - Can do this with fairly ordinary gates,
if you don't care about running in reverse
 - Awkward to scale up

Symmetric Outputs

- Every signal takes **two** lines
 - Fanout == 1
 - Output logic 0 is {0,1}, logic 1 is {1,0}
 - A lot of extra wires...
 - Can be applied to conventional gates if you don't need to run in reverse


Billiard-Ball Conservancy

- Number of 1's input == 1's output
 - Fanout == 1
 - Requires special gates, e.g., **CSWAP**, **Conditional SWAP**, aka **Fredkin** (which is also known as a Fredkin gate)
 - Easily reversible execution

CSWAP (Fredkin) Gate

- CSWAP (S, A, B) is $\{ (S ? B : A) , (S ? A : B) \}$

S	A	B		QA	QB
0	0	0		0	0
0	0	1		0	1
0	1	0		1	0
0	1	1		1	1
1	0	0		0	0
1	0	1		1	0
1	1	0		0	1
1	1	1		1	1

 

CSWAPs in Verilog

- Verilog modeling of CSWAP
 - *Sequence* of gate operations
 - Make and use a **CSWAP** macro:

```
`define CSWAP(S,A,B) {A,B}=(S?{B,A}:{A,B})
```
 - No assignments outside the macro except initialization, no repeated operands
 - Goal: same function, minimum ancilla with unit fanout (*sequential reuse* is OK)
- Here is a 1-bit Full Adder using CSWAP:
<https://aggregate.org/QC/cswapfa.html>

How To Copy A Value?

- `copy=0 ;`
`notcopy=1 ;`
``CSWAP (S , copy , notcopy) ;`

Note that this also makes complement...
but `copy` and `notcopy` are essentially ancilla

Your Project

- Start with the SITE code:
<https://aggregate.org/QC/sitemul.html>
- That code uses a big array of bits and creates a new bit for each result... CSWAP doesn't
- Rewrite `module mul` so it uses only CSWAP
 - Use as few CSWAP as possible
 - Use as few ancilla as possible